

11508/21508

Roll No. _____

Total No. of Pages: 3

11508/21508

B. Tech. I - Sem. Main/Back & II-Sem. Back Exam., March – 2021
1FY3-08 /2FY3-08 Basic Electrical Engineering

Time: 2 Hours

Maximum Marks: 80
Min. Passing Marks:

Instructions to Candidates:

Part – A: Short answer questions (up to 25 words) 5×2 marks = 10 marks.
All five questions are compulsory.

Part – B: Analytical/Problem solving questions 4×10 marks = 40 marks.
Candidates have to answer four questions out of six.

Part – C: Descriptive/Analytical/Problem Solving questions 2×15 marks = 30 marks.
Candidates have to answer two questions out of three.

Use of following supporting material is permitted during examination.
(Mentioned in form No. 205)

1. NIL

2. NIL

PART – A

- Q.1 Define ideal voltage and current source. [2]
- Q.2 Define effective value of A.C. quantity. [2]
- Q.3 Write down the components of no load current of a transformer. [2]
- Q.4 What is synchronous motor? Classify it on the basis of rotor. [2]
- Q.5 What is power transistor? [2]

PART - B

Q.1 Frame and solve the node equations of the network shown in figure1. Find out the current following in each branches. [10]

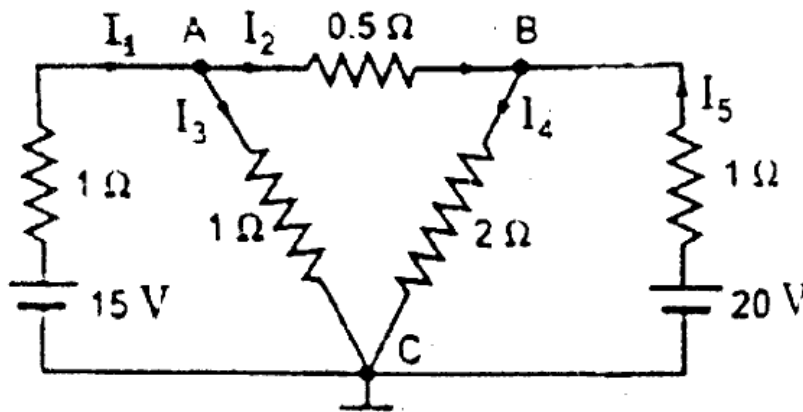


Figure 1

Q.2 Find the RMS value, average value and the form factor of the voltage waveform shown in figure2. [10]

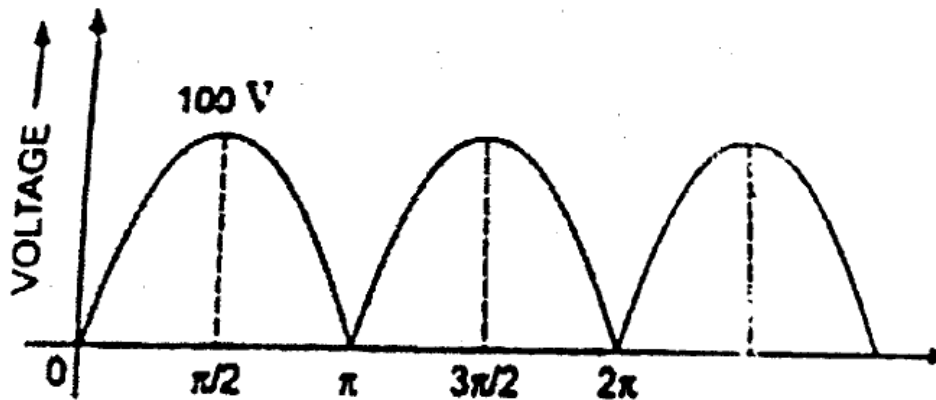


Figure 2

Q.3 Draw and explain simplified equivalent circuit diagram of transformer. [10]

Q.4 Explain Double Revolving Field theory. [10]

Q.5 What is chopper? Classify it and differentiate it with inverter. [10]

Q.6 How power is measured in electrical installation? Describe different methods in brief. [10]

PART - C

- Q.1 (a) Find the current following through $2\ \Omega$ resistor across branch AB in the circuit, shown in figure 3 using Thevenin's theorem. [9]

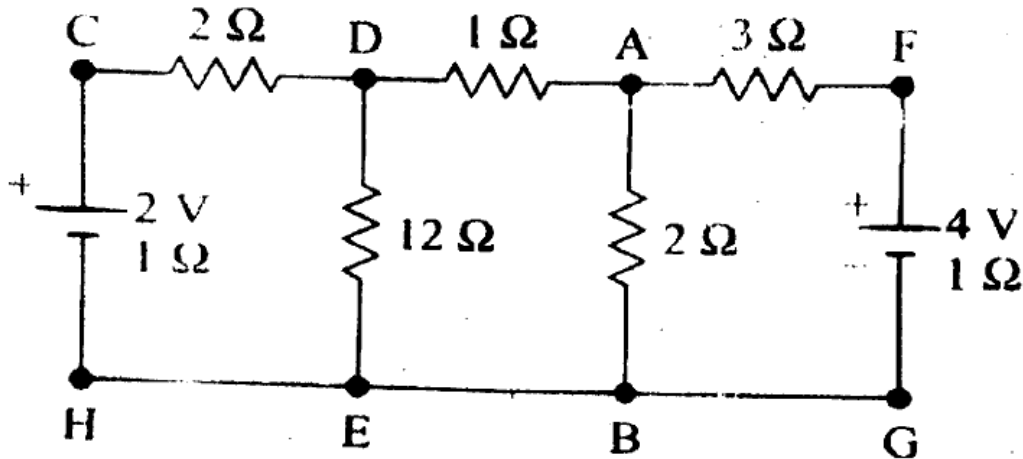


Figure 3

- (b) Derive the expression for EMF equation of the transformer. [6]
- Q.2 (a) Explain acceptor and rejector circuit and compare them. [9]
- (b) What is IGBT? Draw and explain its VI characteristics. [6]
- Q.3 (a) Explain speed control methods of separately excited DC motor. [5]
- (b) A 50kW, 400V, three phase synchronous machine is operating at full load with an efficiency of 92%. If the field current is adjusted to make its power factor 0.8 leading, estimate the armature current. [5]
- (c) Compare SFU, MCB and MCCB. [5]

<https://www.btubikaner.com>

Whatsapp @ 9300930012

Send your old paper & get 10/-

अपने पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से