

Roll No.

Total Page No. : 4

41N0701

41N0701

**B.TECH. IV SEM MAIN/BACK EXAM
AUGUST-2023
ELECTRONICS AND COMMUNICATION
ENGINEERING
(4EC4-01) - APPLIED ELECTRONICS**

Time : 3 Hours]

[Max. Marks : 70

[Min. Passing Marks :

Instructions to Candidates : Part – A : Short answer type questions (up to 25 words)

10 × 2 marks = 20 marks. All ten questions are compulsory.

Part – B: Analytical/Problem Solving questions 5 × 4 marks = 20 marks. Candidates have to answer 5 questions out of 7.

Part – C: Descriptive/Analytical/Problem Solving questions 3 × 10 marks = 30 marks. Candidates have to answer 3 questions out of 5.

Schematic diagrams must be shown wherever necessary. Any data you feel missing may suitably be assumed and stated clearly. Units of quantities used/calculated must be stated clearly.

Use of following supporting materials is permitted during examination. (Mentioned in form No. 205)

1 _____

2 _____

PART A

1. ✓ What is feedback in amplifiers ? [2]
2. How does the high-frequency response of a CE (Common Emitter) stage differ from its low-frequency response ? [2]
3. Define the Gain Bandwidth Product of an amplifier and explain its significance. [2]
4. ✓ What are Crystal Oscillators, and why are they widely used for high-precision oscillations ? [2]

Z-471


(1)

P.T.O.

5. What is the advantage of using transformer for a Class A amplifier ? [2]
6. Describe the working principle of Class B/AB Push-Pull Amplifiers and their benefits. [2]
7. Why are heat sinks essential in power amplifiers, and how do they improve thermal management ? [2]
8. What is Efficiency in amplifiers, and how can it be calculated ? [2]
9. Explain the Barkhausen Criterion for sustained oscillations in feedback systems. [2]
10. Define Power Output in amplifiers and explain its relationship with load impedance. [2]

PART B

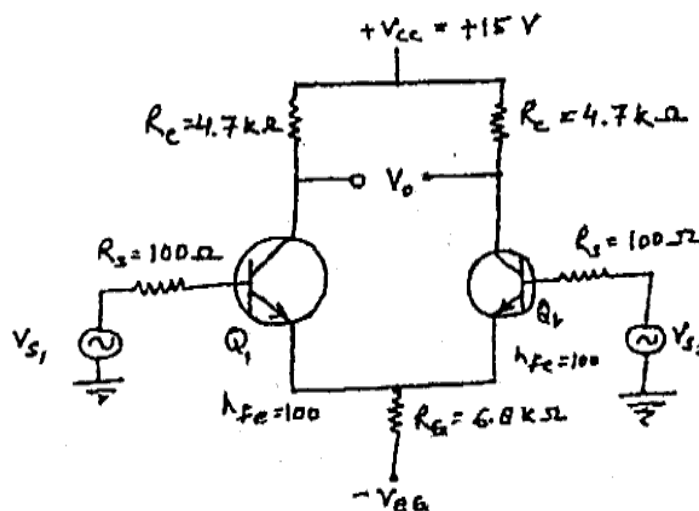1. Prove that the maximum efficiency of class A transformer coupled amplifier is 50% and that of class B type is 78.5%. [4]
2. Draw the circuit of push pull class B amplifier coupled using transformers and explain the operation. Prove that all the even harmonics get eliminated. What is the assumption made for this ? [4]
3. What are the main factors to consider while designing and tuning Sinusoidal Oscillators for specific applications ? <https://www.btubikaner.com> [4]
4. How do you analyze multistage amplifiers at high frequencies, and what challenges may arise in such analysis ? [4]
5. How do Class C Power Amplifiers operate, and what are their main applications ? [4]
6. Draw the circuit of BJT Wien bridge oscillator and explain its working ? [4]
7. For the given Figure dual input, balanced output differential amplifier configuration. Assuming silicon transistors with $h_{ie} = 2.8k \Omega$. [4]




Calculate

- Operating point values
- Differential gain
- Common mode gain
- CMRR
- Output if $V_{s1} = 70$ mV peak to peak at 1KHz and $V_{s2} = 40$ mV peak to peak at 1kHz.

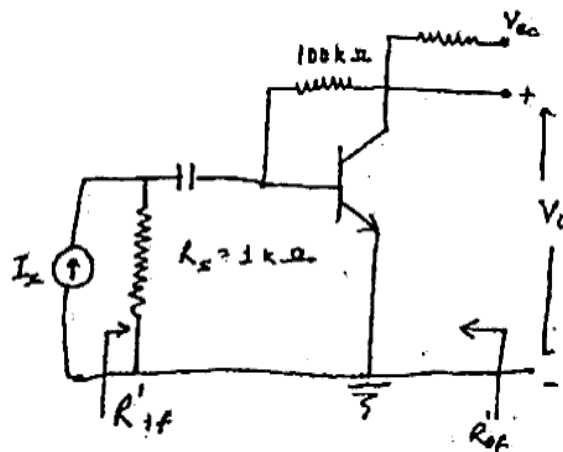PART C

- Distinguish between voltage series feedback and current series feedback. Explain briefly with suitable circuit diagrams. [10]
- What is monostable multivibrator ? Explain its working with the help of neat waveforms. [10]
- Explain the concepts of Crossover Distortion and Harmonic Distortion in power amplifiers. [10]
- What is a Class B/AB Push-Pull Amplifier, and why is it commonly used in audio applications ? [10]
- For the given feedback amplifier circuit, $h_{fe} = 100$, $h_{ie} = 1$ k Ω and neglect h_{re} and h_{oe} . Find :



- $R_{mf} = V_o/I_s$ where $I_s = V_s/R_s$
- $A_{vf} = V_o/V_s$
- R_{if}
- R'_{of}

<https://www.btubikaner.com>

Whatsapp @ 9300930012

Send your old paper & get 10/-

अपने पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से
