

310605	Roll No. _____	Total No of Pages: 4
	310605 B. Tech. III - Sem. (Main) Exam., February - 2021 Electrical Engineering 3EE4-05 Electrical Circuit Analysis Common for EE/EEE	

Time: 3 Hours

Maximum Marks: 120

Instructions to Candidates:

Part – A: Short answer questions (up to 25 words) 10×2 marks = 20 marks.
All ten questions are compulsory.

Part – B: Analytical/Problem Solving questions (up to 100 words) 5×8 marks = 40 marks. Candidates have to answer five questions out of seven.

Part – C: Descriptive/Analytical/Problem Solving questions 4×15 marks = 60 marks.
Candidates have to answer four questions out of five.

Schematic diagrams must be shown wherever necessary. Any data you feel missing may suitably be assumed and stated clearly. Units of quantities used/calculated must be stated clearly.

Use of following supporting materials is permitted during examination.
(Mentioned in form No. 205)

1. NIL

2. NIL

PART - A

- Q.1 What is the utility of Superposition theorem? [2]
- Q.2 How equivalent impedance is calculated in Thevenin Theorem? [2]
- Q.3 How the RL circuit behaves for the step input? [2]
- Q.4 Distinguish between steady state and transient state. [2]
- Q.5 Why is impedance represented by a complex number? [2]
- Q.6 State the Dot rule for coupled circuits. [2]
- Q.7 What is Laplace transform? Define its applications. [2]

[310605]

Page 1 of 4

[1020]

- Q.8 How the RLC series circuit behaves for the frequencies above and below resonant frequencies? [2]
- Q.9 Define transfer impedance and admittance. [2]
- Q.10 What are the assumptions made in the analysis of two-part networks? [2]

PART – B

- Q.1 What is the power loss in the 10Ω resistor in the network shown in Fig.1? Use mesh method. [8]

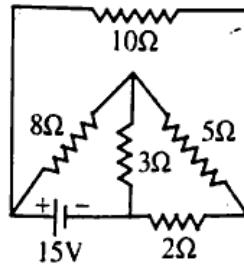


Fig.1

- Q.2 State and explain Compensation theorem. [8]
- Q.3 A resistance R and $5\mu\text{F}$ capacitor are connected in series across a 100V d.c. supply. Calculate the value of R such that the voltage across the capacitor becomes 50V in 5sec after the circuit is switched on. [8]
- Q.4 For a circuit, the applied voltage is $V=622 \sin(2500t + 170^\circ)$ volts, and the resulting current is $i=31 \sin(2500t-145^\circ)$ amperes. Calculate the circuit constants and draw the phasor and impedance diagrams. [8]
- Q.5 A two mesh network is shown in Fig.2. Obtain the expression for $I_1(s)$ and $I_2(s)$ when the switch is closed - [8]


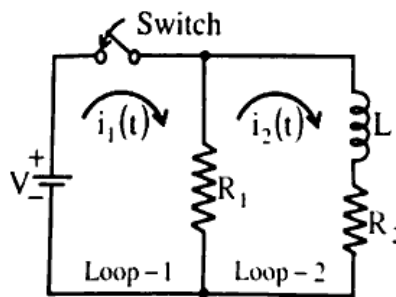


Fig.2


- Q.6 Explain step response of RC series circuit. [8]
- Q.7 Convert the following - [8]
- (a) ABCD parameter into Y-parameter [8]
- (b) h-parameter into Z-parameter

PART - C

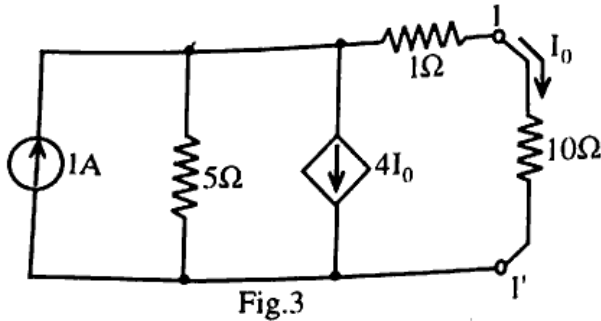
Q.1 Find the power loss in the 10Ω resistor in the circuit of Fig.3 using Norton's theorem - [15]



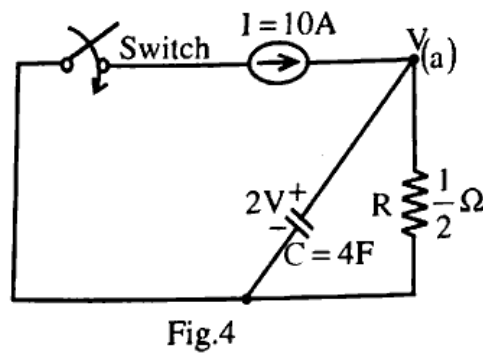Q.2 If $I=10A$, and the switching is done at $t=0$, find $v(t)$ for $t > 0$, if the initial capacitor voltage be $2V$. The circuit is shown in Fig.4 - [15]



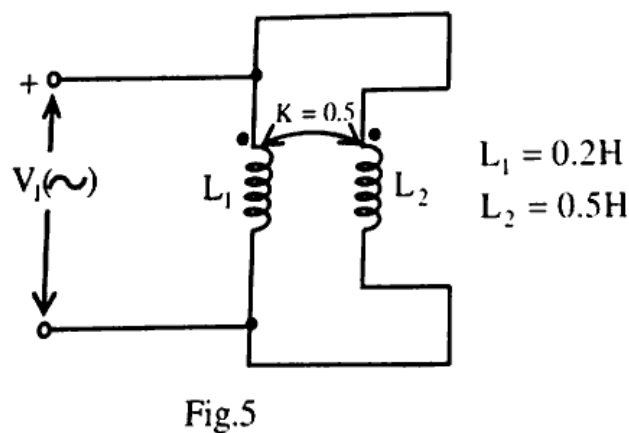Q.3 In the coupled circuit of Figure 5, find the input impedance as well as the net inductance - [15]



Q.4 In the circuit of Figure 6. Obtain expression for the current $i(t)$ when the switch is moved from position (1) to position (2) at $t=0$. Use Laplace transform - [15]

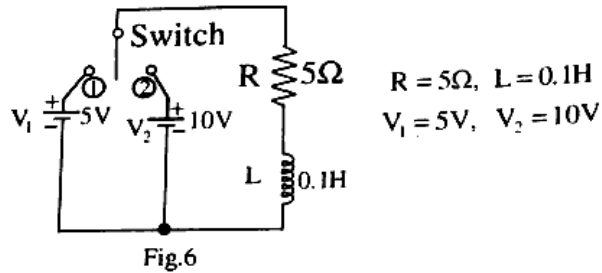


Fig.6

[15]

Q.5 In a two port network -

$$Z_{11}=2\Omega, Z_{12}=Z_{21}=5\Omega, Z_{22}=1\Omega$$

Find -

- (a) Y-parameters
- (b) h-parameters
- (c) ABCD-parameters

<https://www.btubikaner.com>

Whatsapp @ 9300930012

Send your old paper & get 10/-

अपने पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से

Page 4 of 4

[310605]

[1020]