

310804	Roll No. _____	Total No of Pages: 3
	310804 B. Tech. III Sem. (Main) Exam., Dec. - 2019 Common for ECE/EIC 3EI4-04 Digital System Design	

Time: 3 Hours

Maximum Marks: 120

Instructions to Candidates:

Part – A: Short answer questions (up to 25 words) 10×2 marks = 20 marks. All ten questions are compulsory.

Part – B: Analytical/Problem Solving questions 5×8 marks = 40 marks. Candidates have to answer five questions out of seven.

Part – C: Descriptive/Analytical/Problem Solving questions 4×15 marks = 60 marks. Candidates have to answer four questions out of five.

Schematic diagrams must be shown wherever necessary. Any data you feel missing may suitably be assumed and stated clearly. Units of quantities used/calculated must be stated clearly.

Use of following supporting materials is permitted during examination. (Mentioned in form No. 205)

1. NIL

2. NIL

PART - A

Q.1 Evaluate the Boolean function $F = xy + \bar{x}z$ in a product of maxterms. [2]

Q.2 Draw the logic diagram for Boolean expression without simplifying [2]

$$F = (AB + \bar{A}\bar{B})(C\bar{D} + \bar{C}D)$$

Q.3 Show that dual of Ex – OR is equal to its complement. [2]

Q.4 Develop the K – map and solve the Boolean function [2]

$$F(x, y, z) = \sum(2, 3, 4, 5)$$

http://www.mgsuonline.com

http://www.mgsuonline.com

- Q.5 Differentiate flip flop and Latch. [2]
- Q.6 Mealy and Moore's machines can be differentiated on which factors? [2]
- Q.7 Draw C - MOS inverter circuit. [2]
- Q.8 Calculate noise margin for input voltage level 5V and threshold voltage level 4.15V. [2]
- Q.9 Define number of transistor range for SSI, MSI, LSI and VLSI. [2]
- Q.10 Define data type in VHDL. [2]

PART - B

- Q.1 Convert the following numbers in required number system - [8]
- (a) $[643]_{10} \rightarrow [\quad]_{\text{Excess-3}}$
- (b) $[1010111]_{\text{GRAY}} \rightarrow [\quad]_2$
- Q.2 Plot the logical expression $ABCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}C + AB$ on a K - map; obtain the simplified expression from map. http://www.mgsuonline.com [8]
- Q.3 Design a full subtractor and realize it with logic gates. [8]
- Q.4 Construct a parallel binary adder with proper designing methodology. [8]
- Q.5 Realize T flip - flop using S - R flip - flop. [8]
- Q.6 Implement NOR gate using TTL. [8]
- Q.7 Design a state diagram of a circuit to detect the sequence 1011. [8]

PART – C

Q.1 Analyze BCD to Excess – 3 code convertor. [15]

Q.2 How the Race – Round condition is raised? Give solution methodology for this problem. [15]

Q.3 Discuss Pseudo Random Binary sequence generator. [15]

Q.4 Write short note on FPGA. [15]

Q.5 Write VHDL code for MOD – 8 Asynchronous counter using structural modelling. [15]

<http://www.mgsuonline.com>

Whatsapp @ 9300930012

Your old paper & get 10/-

पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से